


# Audio Pitch Shifting and Transmission through Optical Fiber

Emmanuel Havugimana and Wings Yeung

# Motivation


- + Pitch shifting is cool
- + Explore optics
- + Learn to make a PCB board
  - + Less wires and more reliable
  - + Neater
  - + Cool

# 3 Major Components

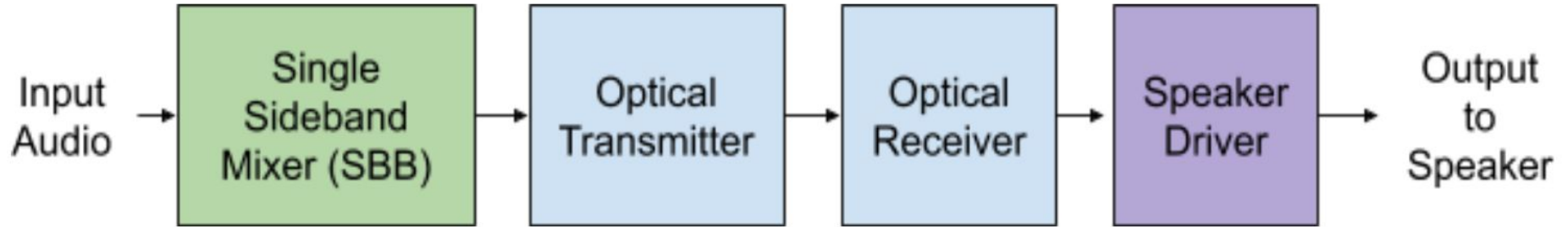

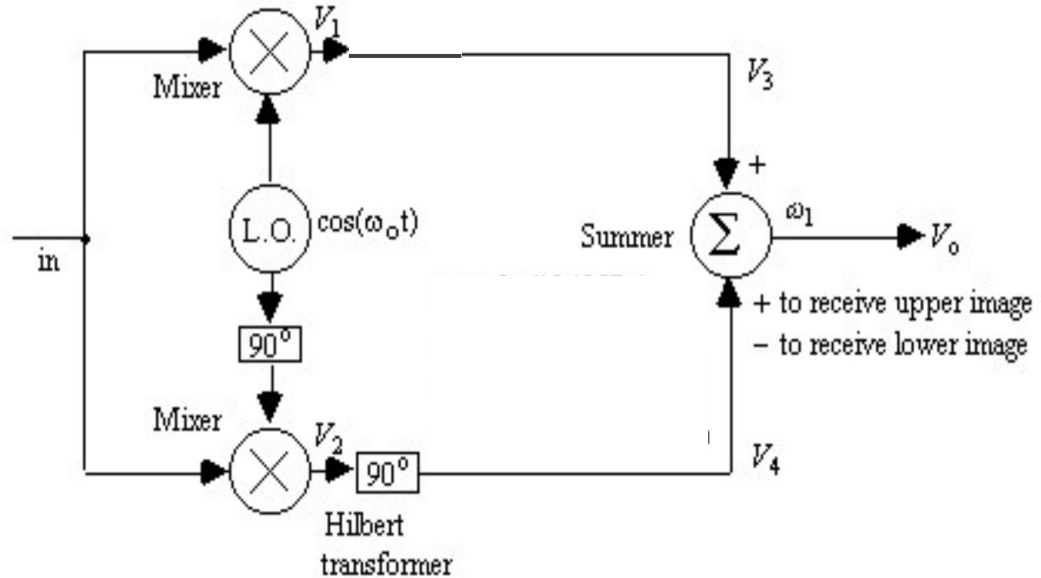
# Single Sideband Mixer (SSB)

- Normal Mixer output sum and differences of input frequencies
- SSB will be used to select output without using filters




# SSB: mixer

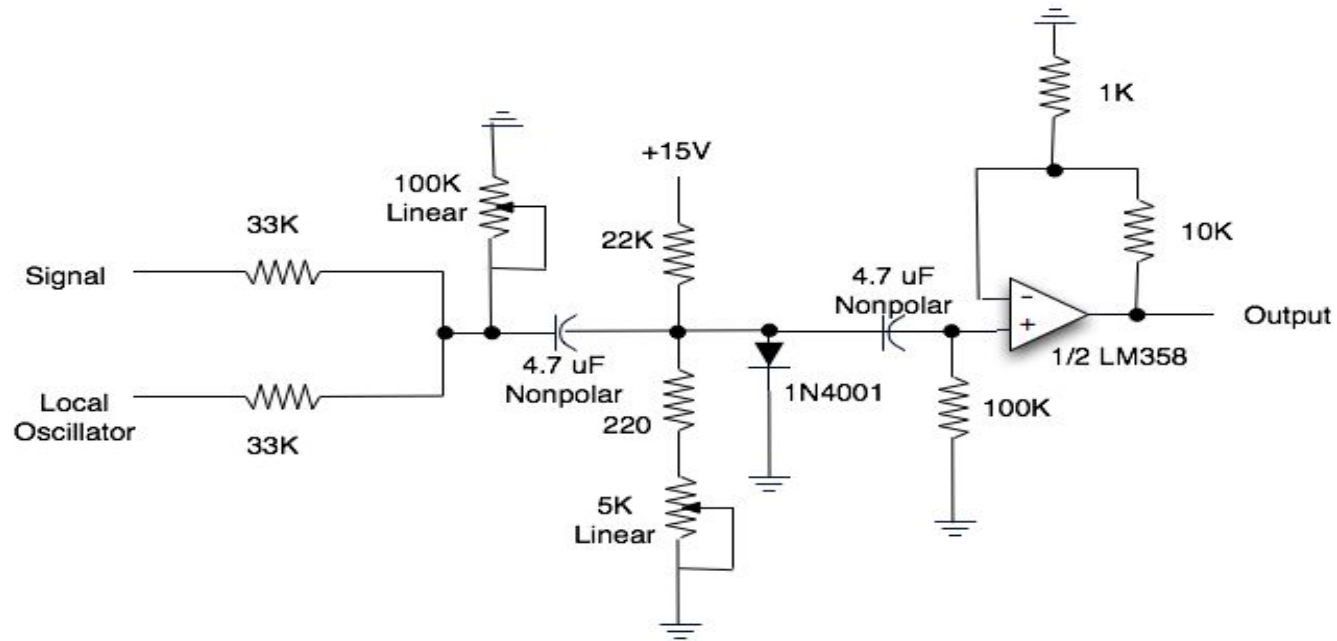

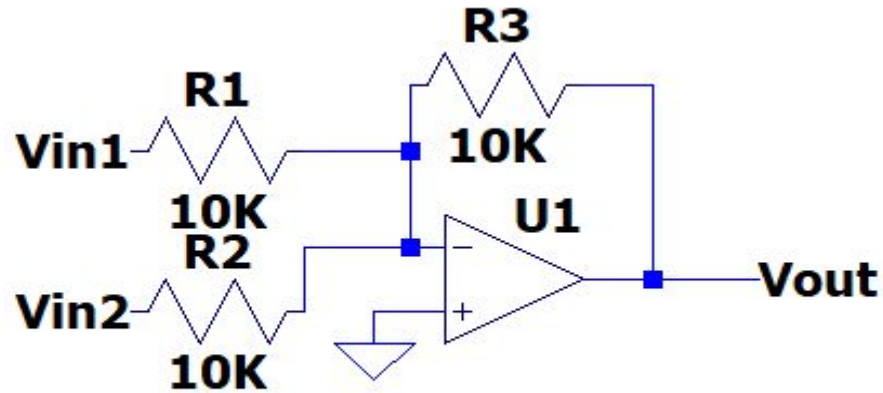
# SSB: Summer

$$V_{out} = -\frac{R_3}{R_1}V_{in1} - \frac{R_3}{R_2}V_{in2}$$



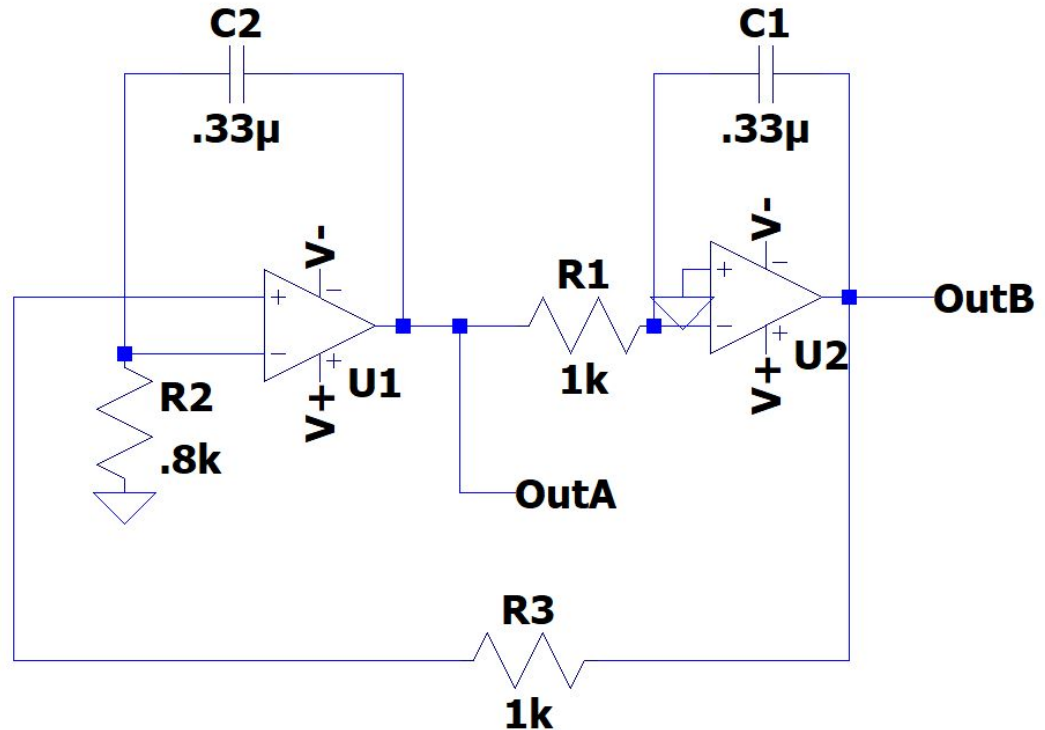
# SSB: Wein Bridge Oscillator

- Outputs both the cosine and the sine waveform
- Vary frequency by changing R1 and R3


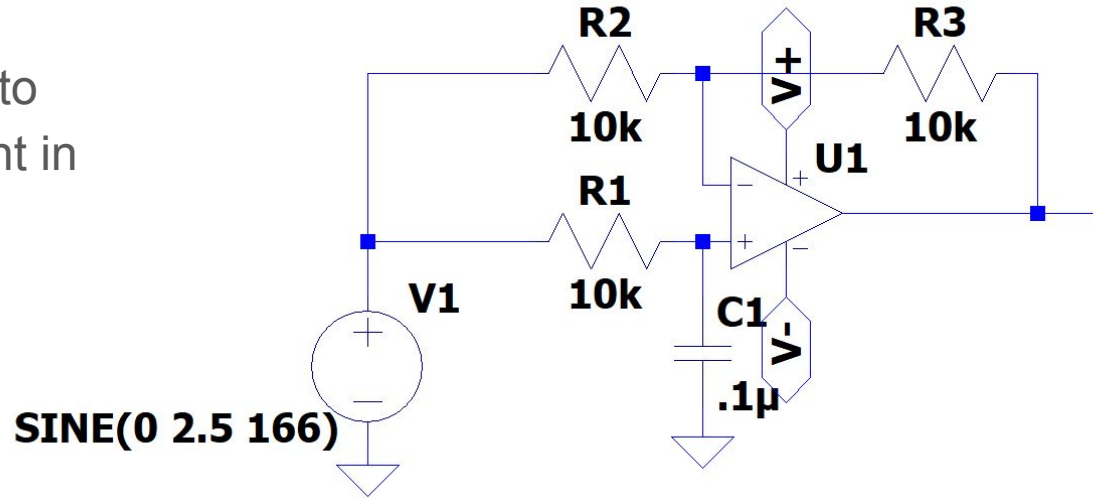
# SSB: 90° Phase Shifter using an All Pass Filter


- Issue: Only works for one specific frequency, therefore, for different frequencies, we need to tune the R1 component in the all-pass filter






# Audio is transmitted and received optically


Optical Transmitter

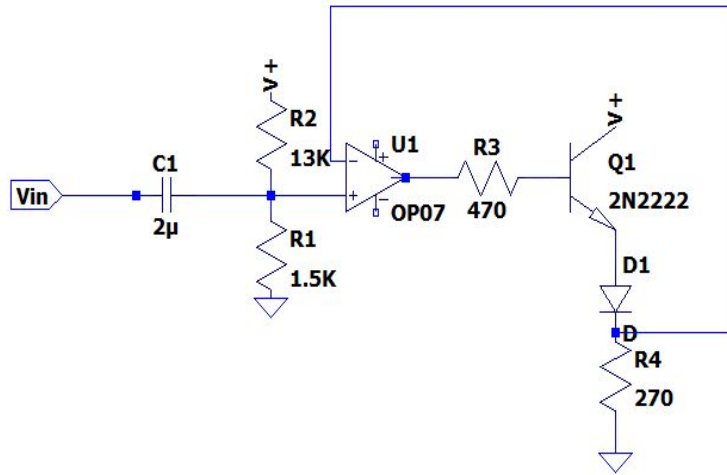


Optical Receiver circuit

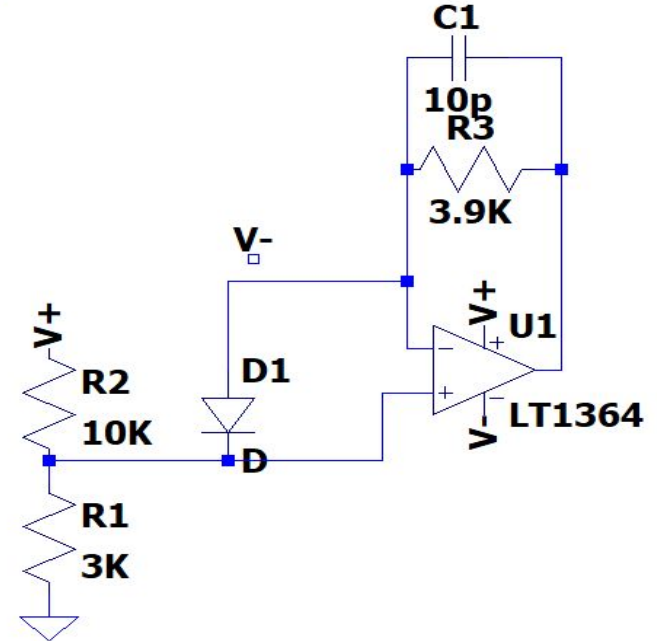

# Speaker Driver from Lab 5

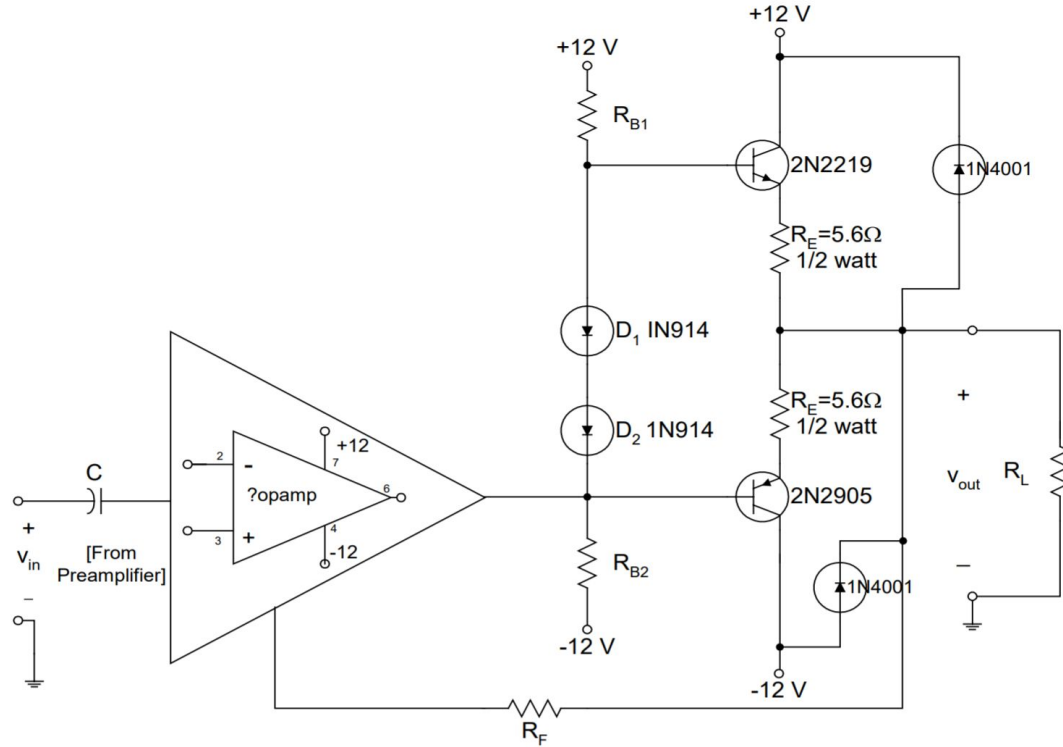

# Timeline

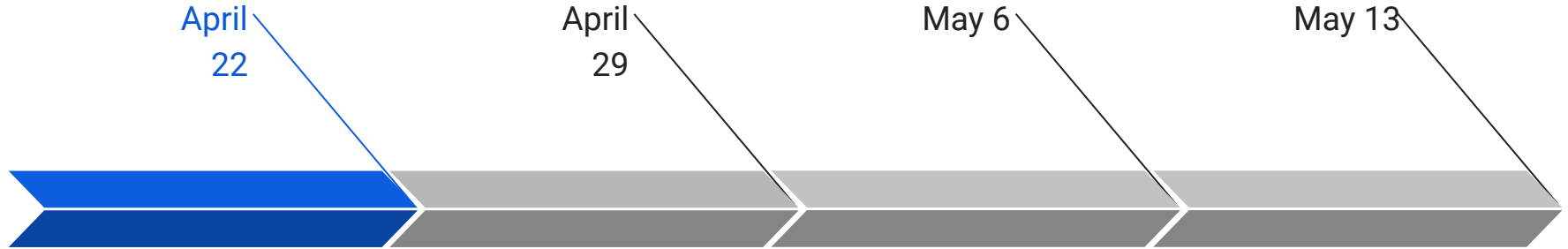

## Optics and Sub-Components

- Test and build optical component
- Build SBB sub components

## SBB and PCB Design

- Put SBB together
- Start PCB design

## Speaker Driver Module

- Finish PCB design and send it in
- Build and test speaker driver

## Finishing Up

- Project Demo
- Write final report

# Summary and Challenges

## Finished

- Sub-components of the SBB filter
- Tested optical fibers

## To Do

- Create speaker driver module
- Put the SBB filter together and test it
- Build PCB board

## Challenges

- Expanding our SBB filter functionality
  - 90 degrees phase shifter that works for a wide band of frequency
  - Putting it all together
- Time constraint due to PCB board